

---

## Table of Contents

.....	1
Introduction .....	1
Part 1 Introduction .....	1
Part 1 Figures and Command Line Outputs .....	1
Part 1 Conclusion .....	9
Part 2 Introduction .....	9
Part 2 Figures and Command Line Outputs .....	9
Part 2 Conclusion .....	13
How part 3 would be implemented .....	13
Part 3 Figures and Command Line Outputs .....	14
Conclusion .....	16

```
clear all
close all
clc

cd code
```

## Introduction

The purpose of assignment 4 is to use modified nodal analysis to simulate the two circuits given to me.

## Part 1 Introduction

For part 1 I created the G and C by performing modified nodal analysis on the circuit given in figure 1 of the assignment. The next objective was to sweep the input voltage from -10V to 10V and plot the output voltage and the voltage at node 3. The next objective was to plot the gain of the circuit in dB as a function of angular frequency. The final objective was to plot the input voltage and output voltage in the time and frequency domain for the following input voltage signals.

- A. A step that transitions from 0 to 1 at 0.03s.
- B. A  $\sin(2\pi f t)$  function with  $f = 1/(0.03)$  1/s. Try a few other frequencies. Comment.
- C. A Gaussian pulse with a magnitude of 1, std dev. of 0.03s and a delay of 0.1s.

## Part 1 Figures and Command Line Outputs


```
cd part1



part1



cd ..



G =
```


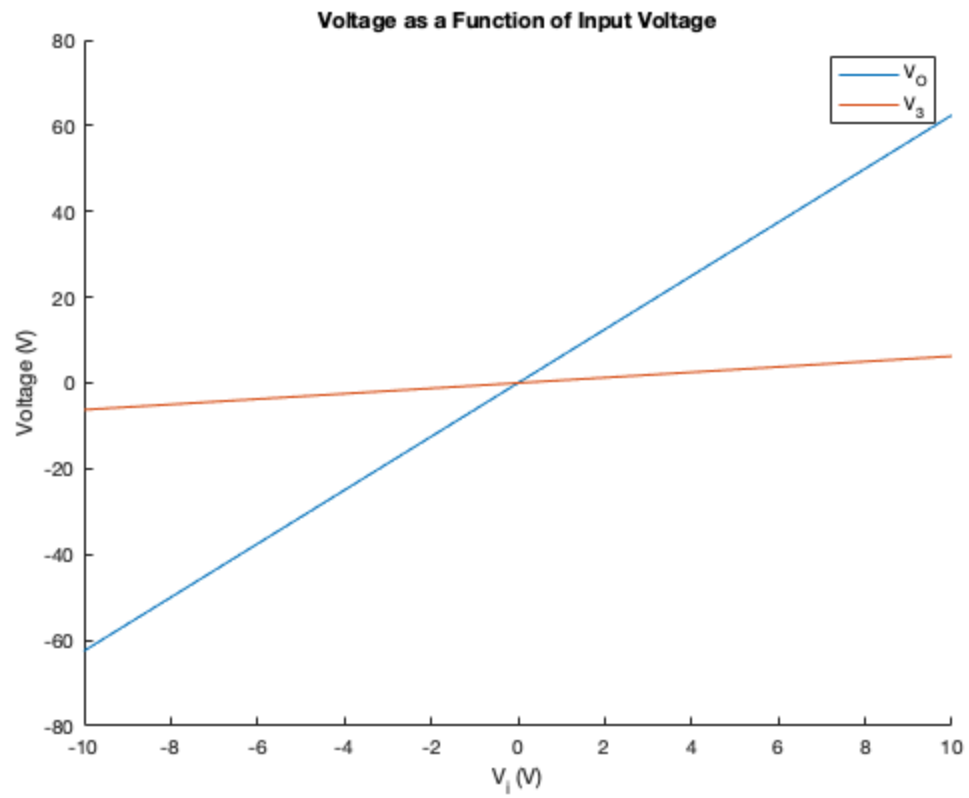
$$C = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1.5 & 0 & 0 \\ 1 & 0 & 0 & 0.1 & 0 \\ -1 & 0 & 0 & -10 & 1 \\ 0 & 0 & 0 & 0 & -10 & 10.001 \\ 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -0.25 & 0.25 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0.2 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$





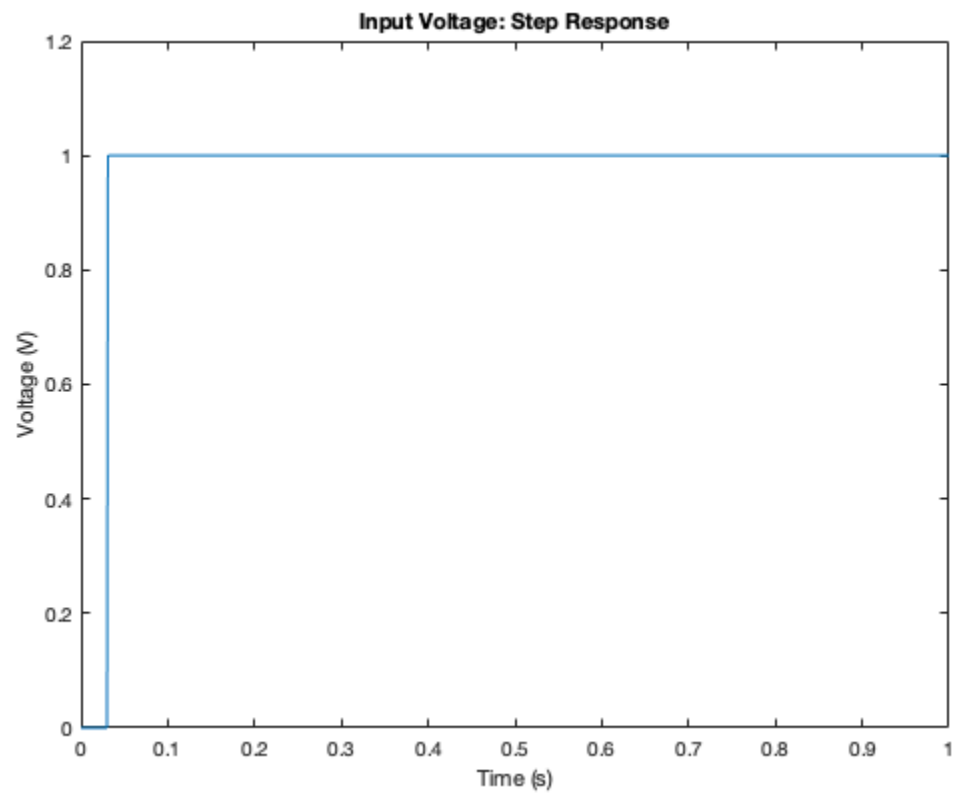
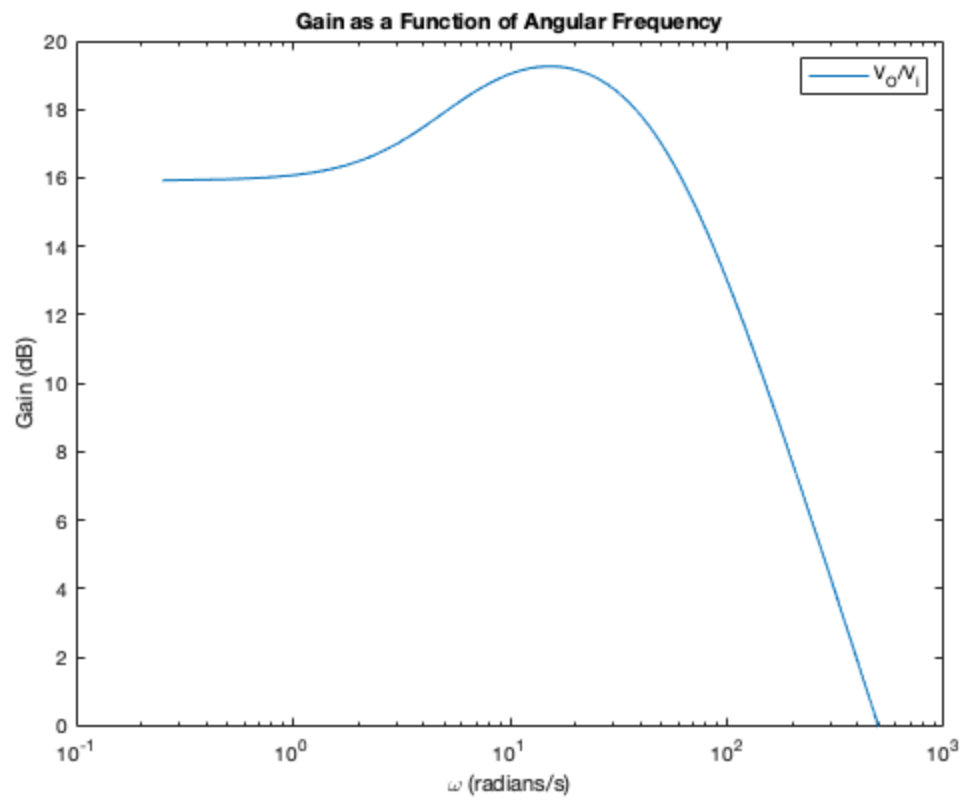


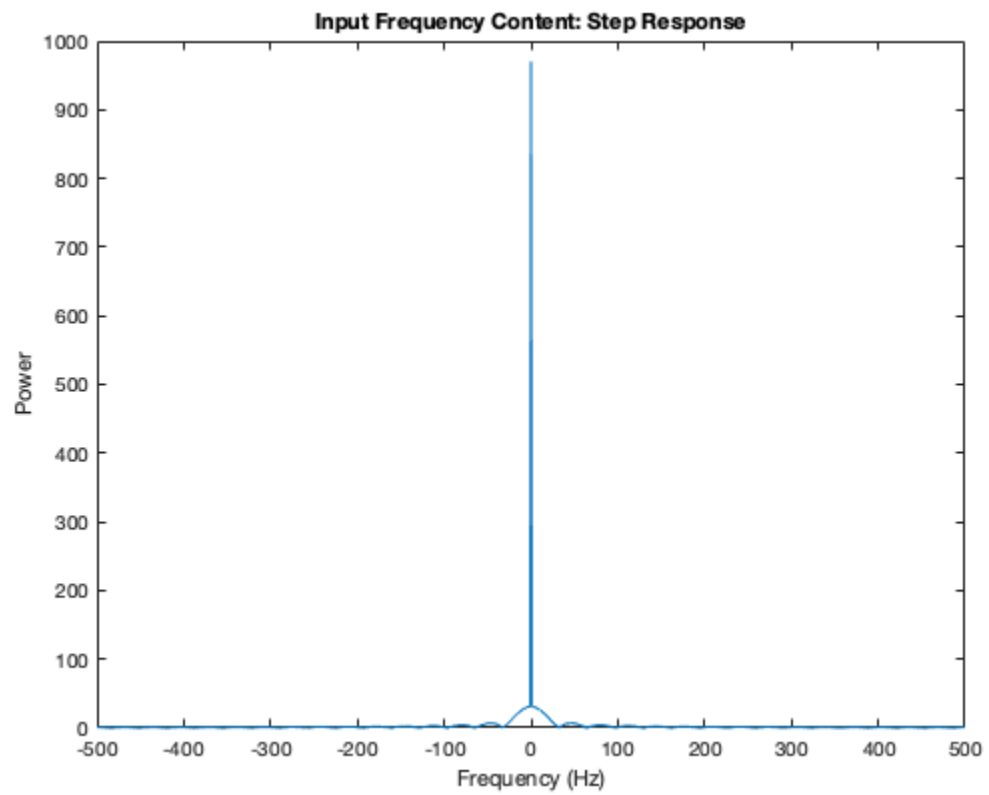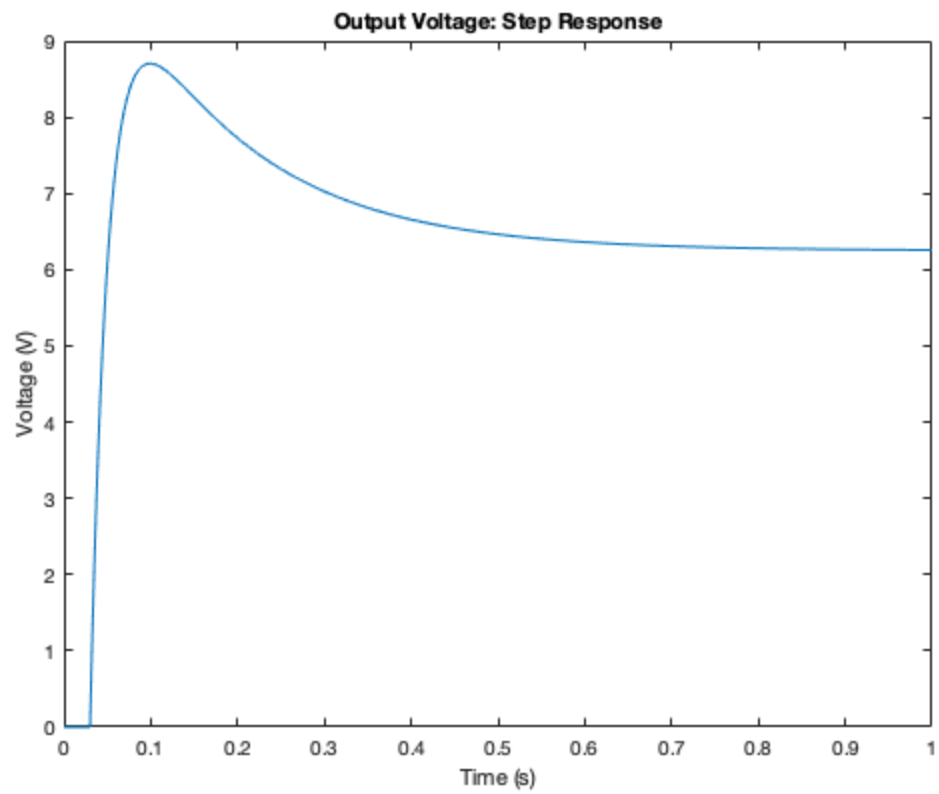

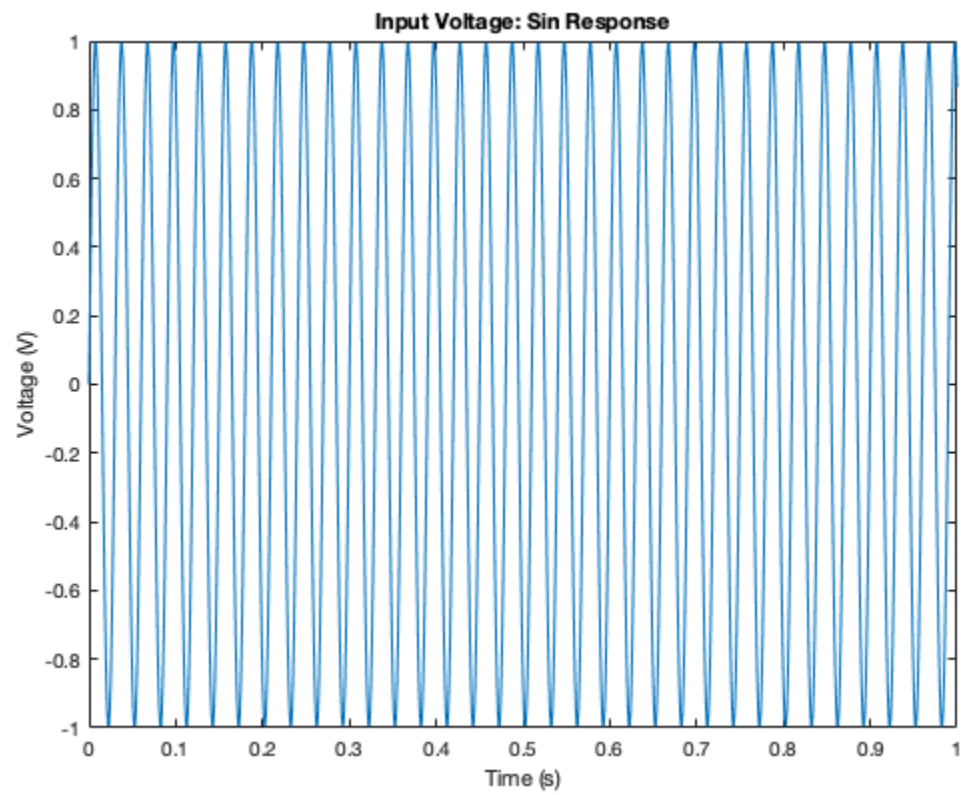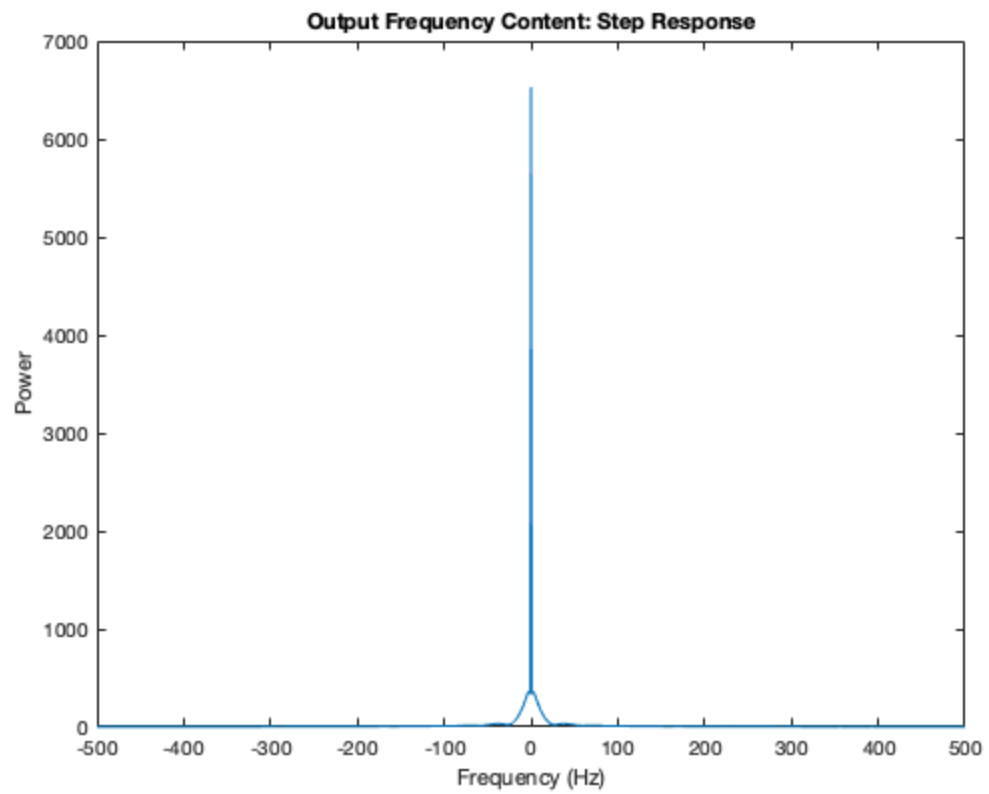


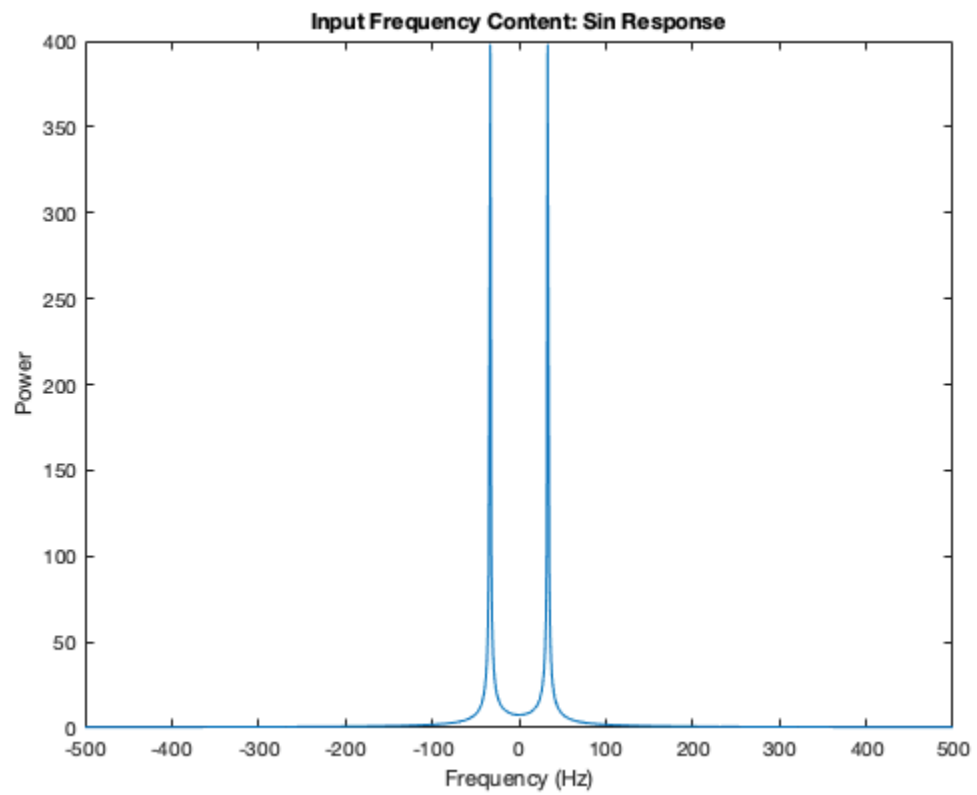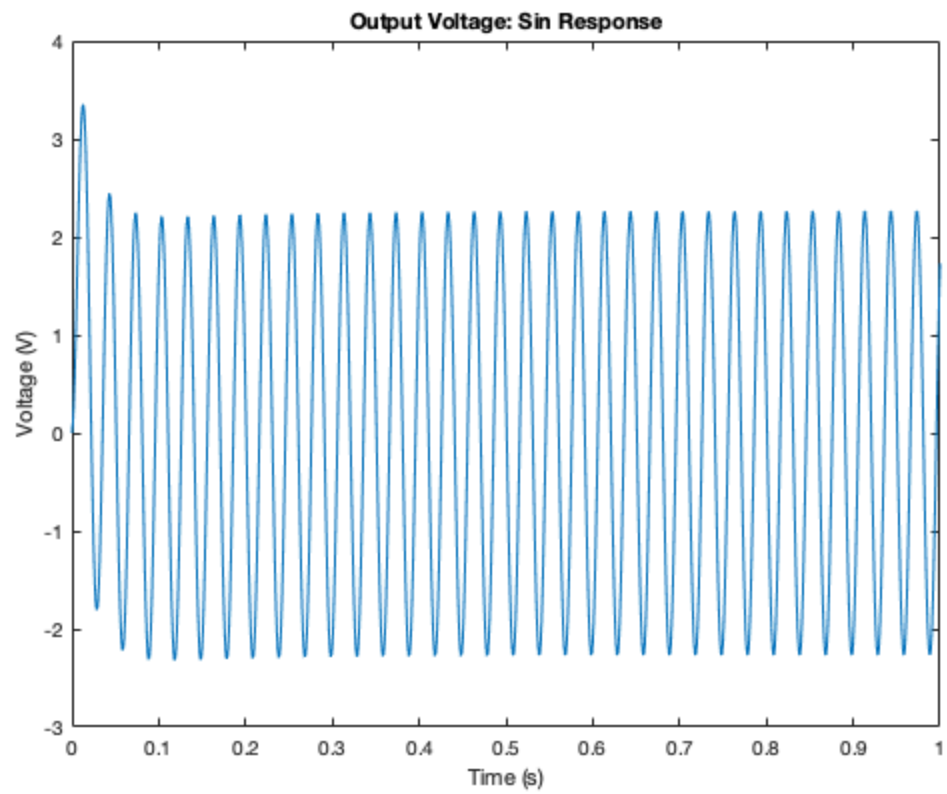

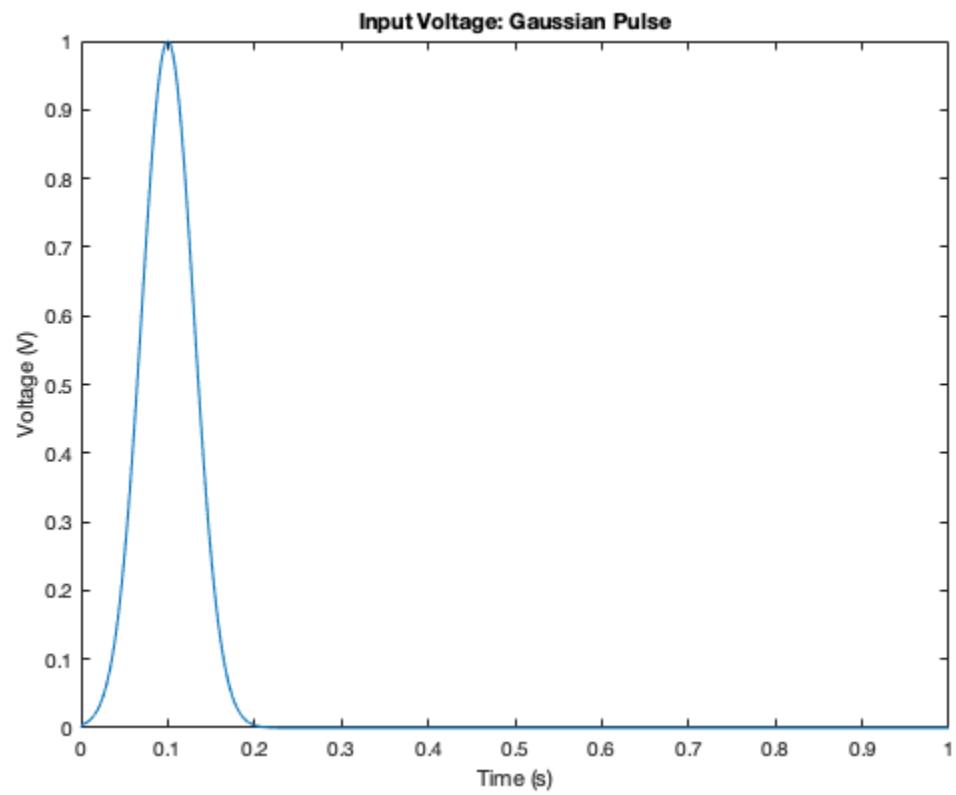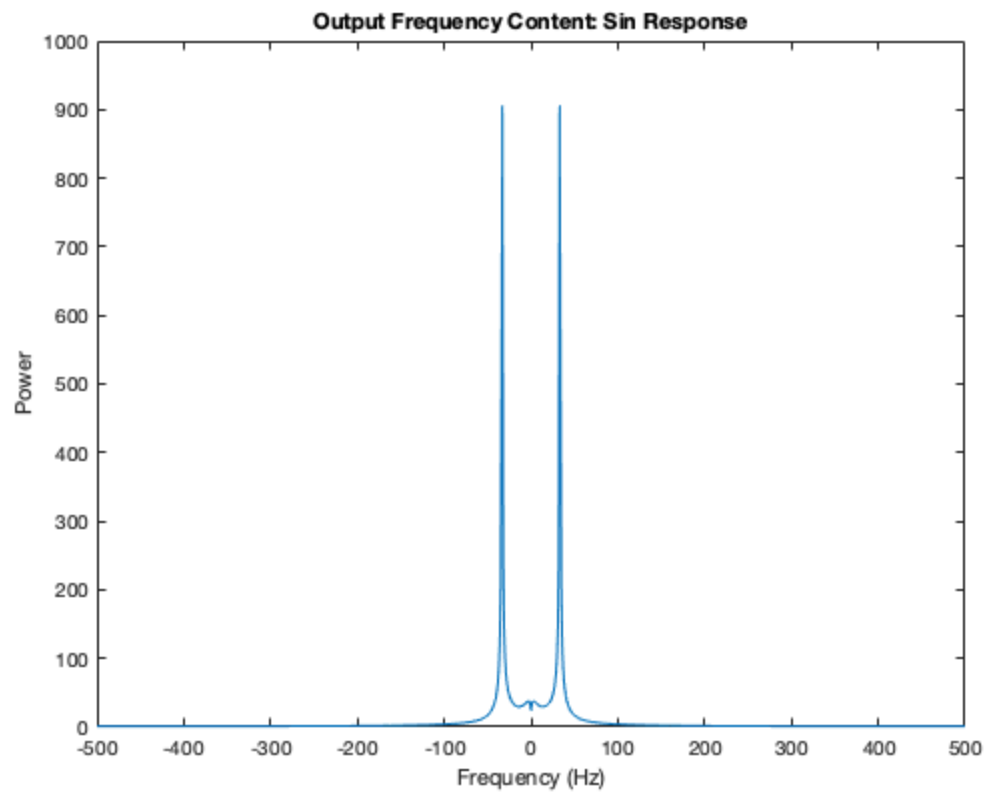

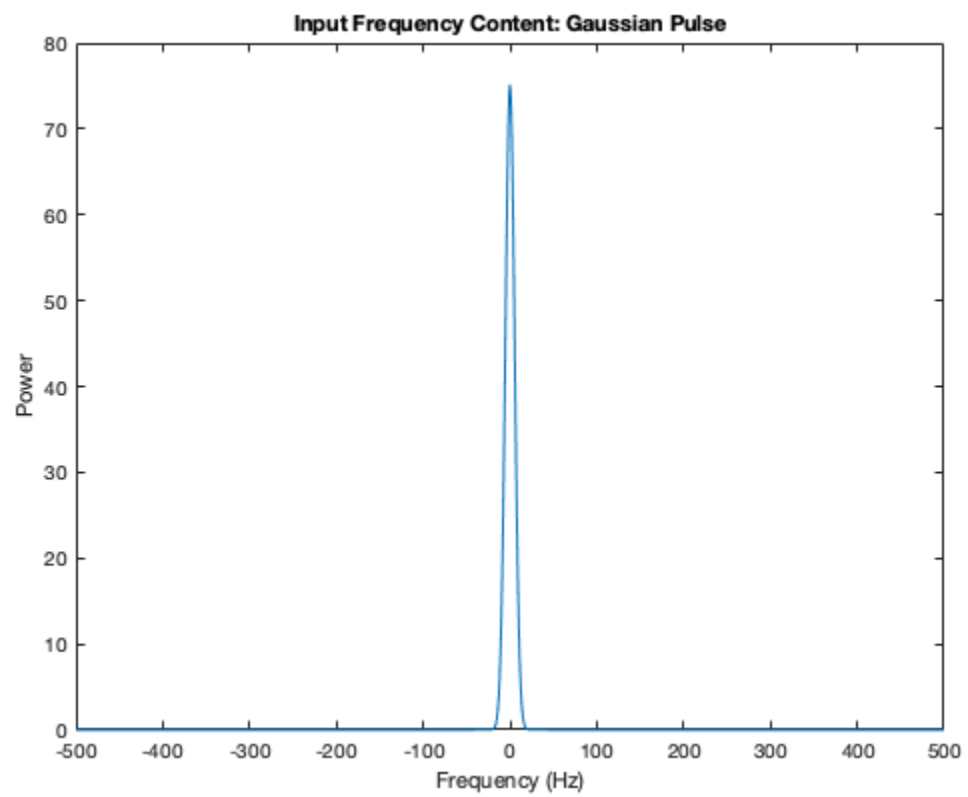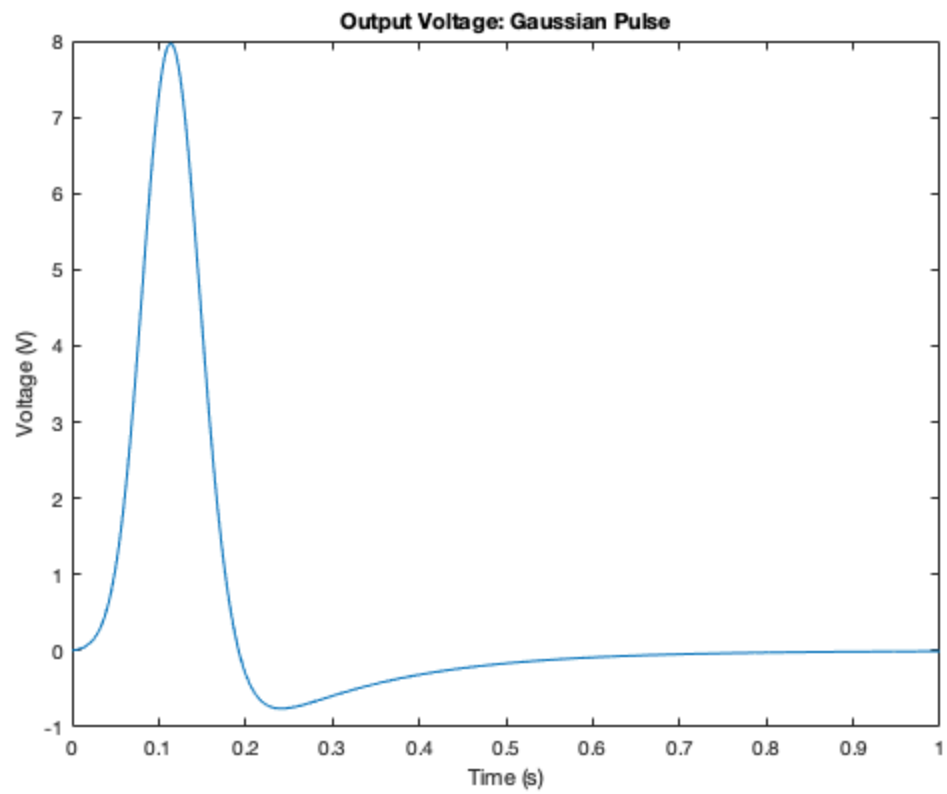



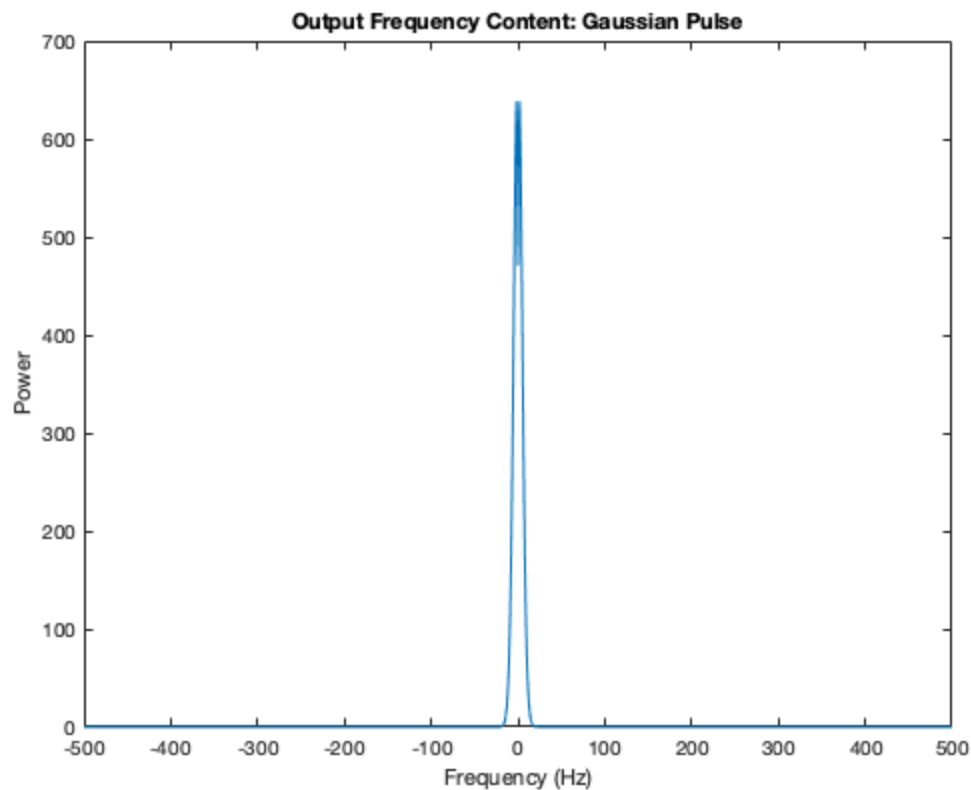

## Part 1 Conclusion

When looking at the gain as a function of angular frequency, it can be concluded that the circuit is a low pass filter. With a low pass filter, you would expect low frequencies to be transmitted and high frequencies to be attenuated. All the plots generated for part one are as expected. When looking at the DC sweep both the output voltage and the voltage at node 3 increase linearly with the input voltage, which makes sense because the circuit is linear.

## Part 2 Introduction

For part 2 I created the G and C by performing modified nodal analysis on the circuit given in figure 2 of the assignment where  $I_n = 0.001 * \text{randn}()$  and  $C_n = 0.00001$ . The next objective was to plot the input voltage and output voltage in the time and frequency domain for a Gaussian pulse input voltage. 3 Plots of the output voltage with different values of  $C_n$  were created. Final 3 Plots of the output voltage with different time steps were created.

## Part 2 Figures and Command Line Outputs

```
cd part2
```


```
part2
```



```
cd ..
```



```
C =
```


---

	0	0	0	0	0
0	-0.25	0.25	0	0	0
0	0	0	1e-05	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0.2					

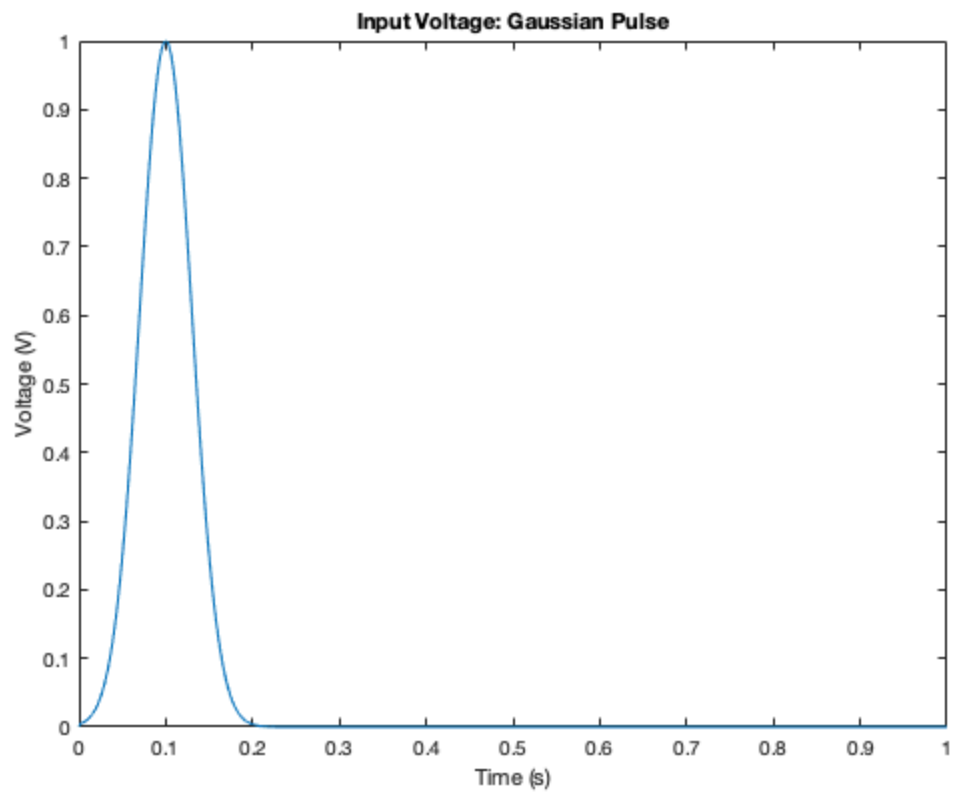

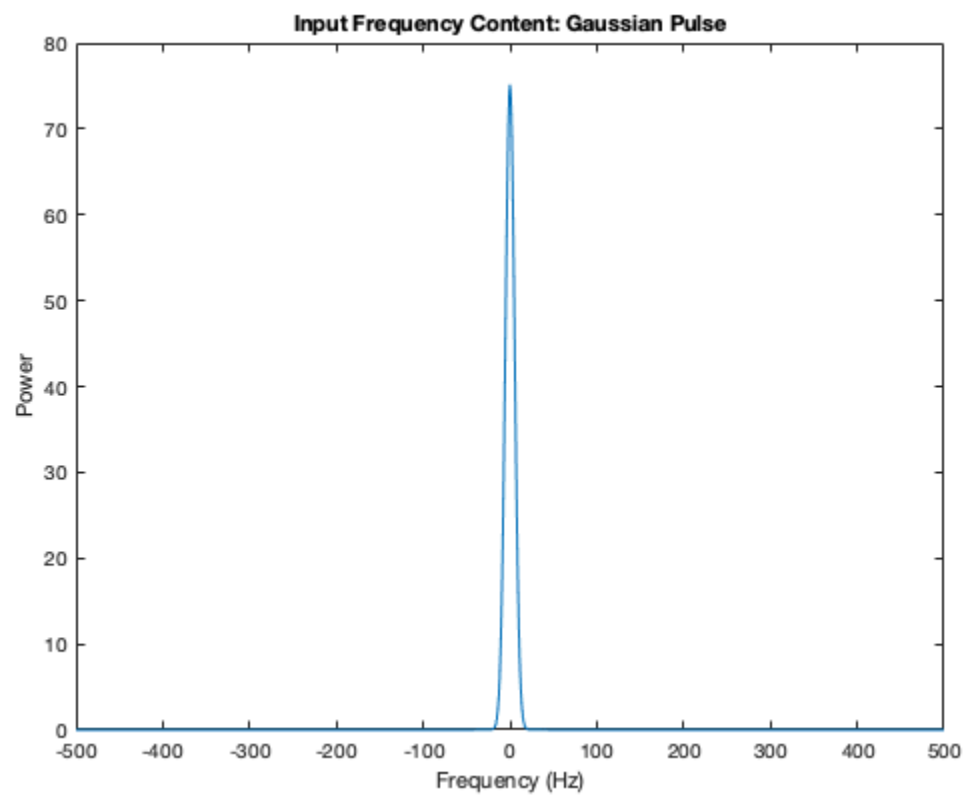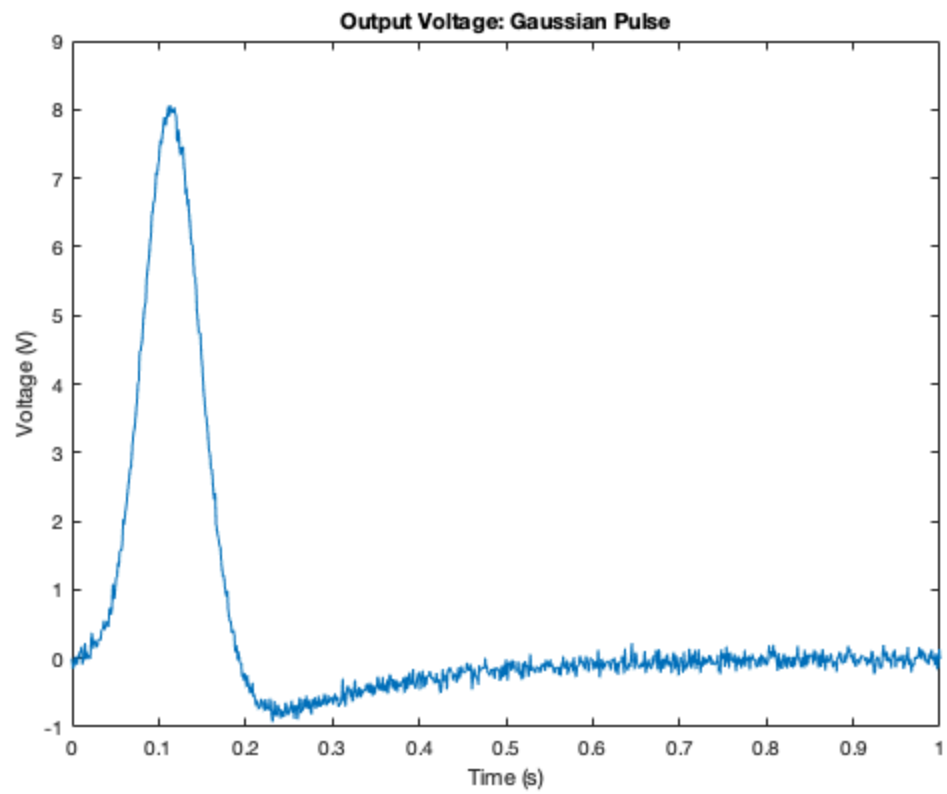

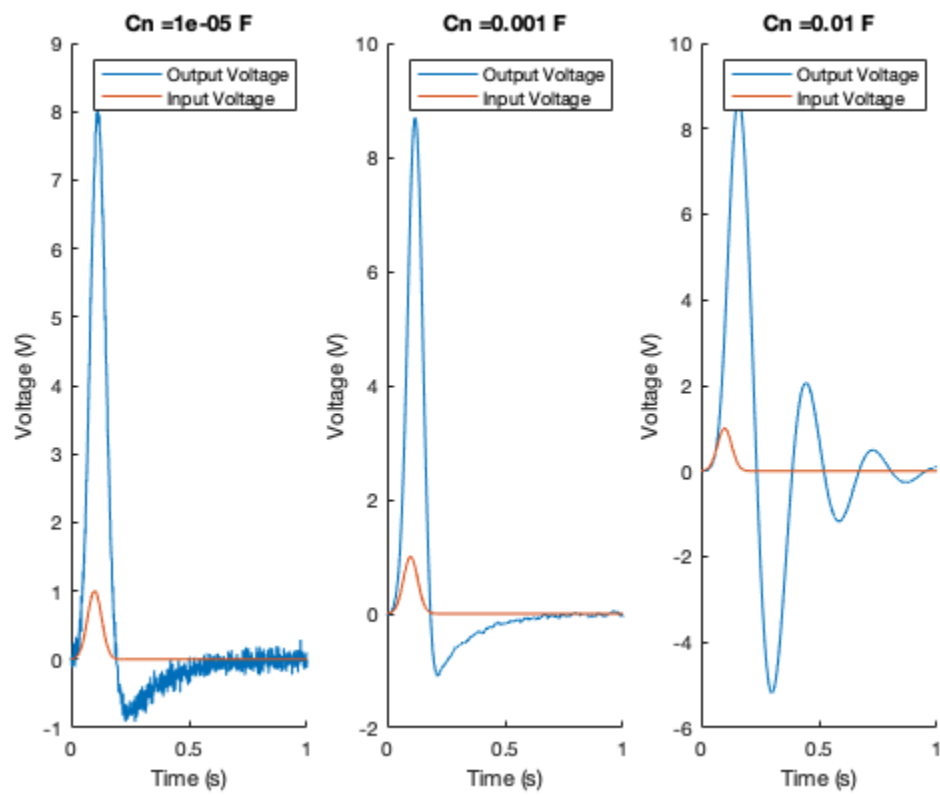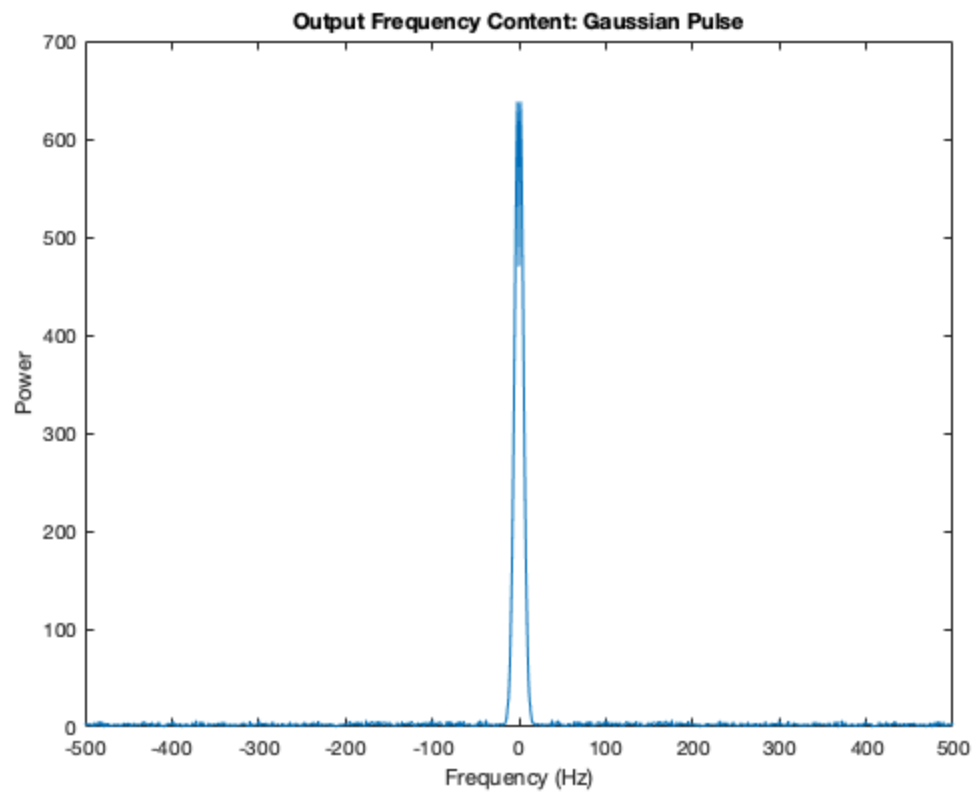

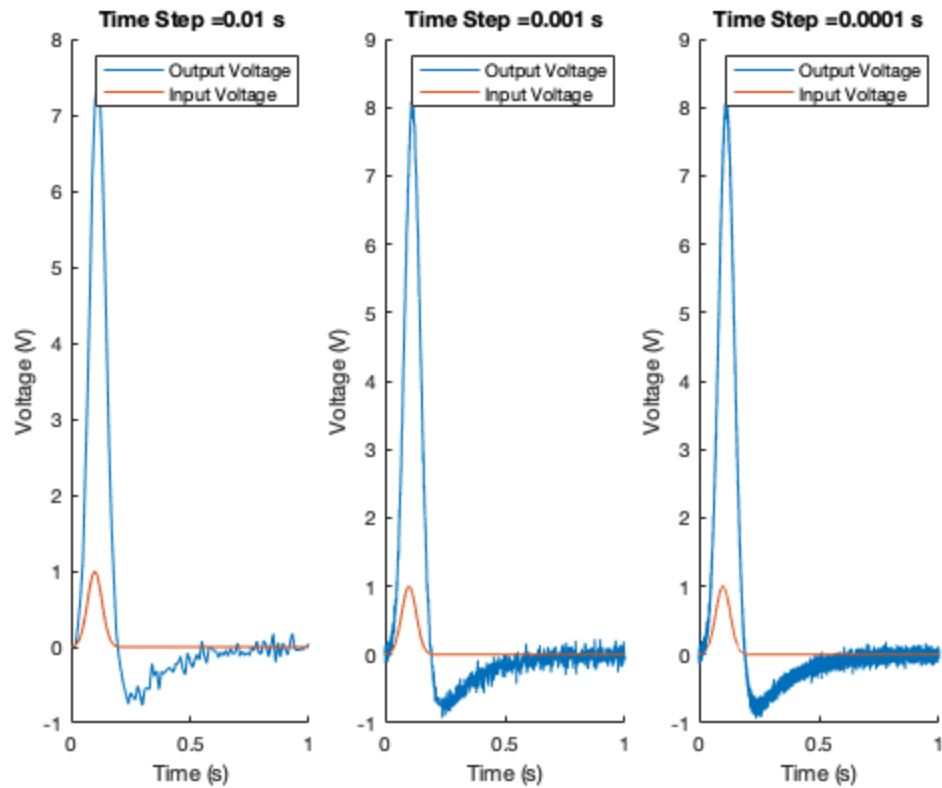

## Part 2 Conclusion

The results of part two are as expected. When a capacitor ( $C_n$ ) and current source ( $I_n$ ) were added to the circuit in parallel with  $R_3$  thermal noise was visible in the output signal frequency and time domain representation. When the value of  $C_n$  has increased the bandwidth of the noise was seen to decrease. One of the effects of increasing the time step is that the output signal becomes more distorted. This means to perform the best analysis a small time step should be used. Another effect of increasing the time step is that the current of  $I_n$  changes less frequently meaning less thermal noise is visible.

## How part 3 would be implemented

The first step would be to add the none linear parts of the circuit into a matrix called  $B$  so that the final equation for the circuit can be written in the form

$$C \frac{dV}{dt} + G\hat{V} + \hat{B}(\hat{V}) = \hat{F}(t)$$

Next, you need to form the Jacobian ( $J$ ) which is the partial derivative of each of the equations in the  $B$  matrix with respect to the variables in the  $V$  matrix.

Next, rearrange the equation and put the matrix in the form as shown below

$$\left(\frac{\widehat{C}}{\Delta t} + \widehat{G}\right) \widehat{V}_n - \frac{C}{\Delta t} \widehat{V}_{n-1} - \widehat{B}(\widehat{V}) - \widehat{F}(t) = 0$$


Using the above equation, the Jacobian, and Newton Raphson method the voltage at each time step can be solved for. The plot of the output and input signal in the time and frequency domain are given below for a sin wave.



## Part 3 Figures and Command Line Outputs


```
cd part3
```

```
part3
```

```
cd ..
```

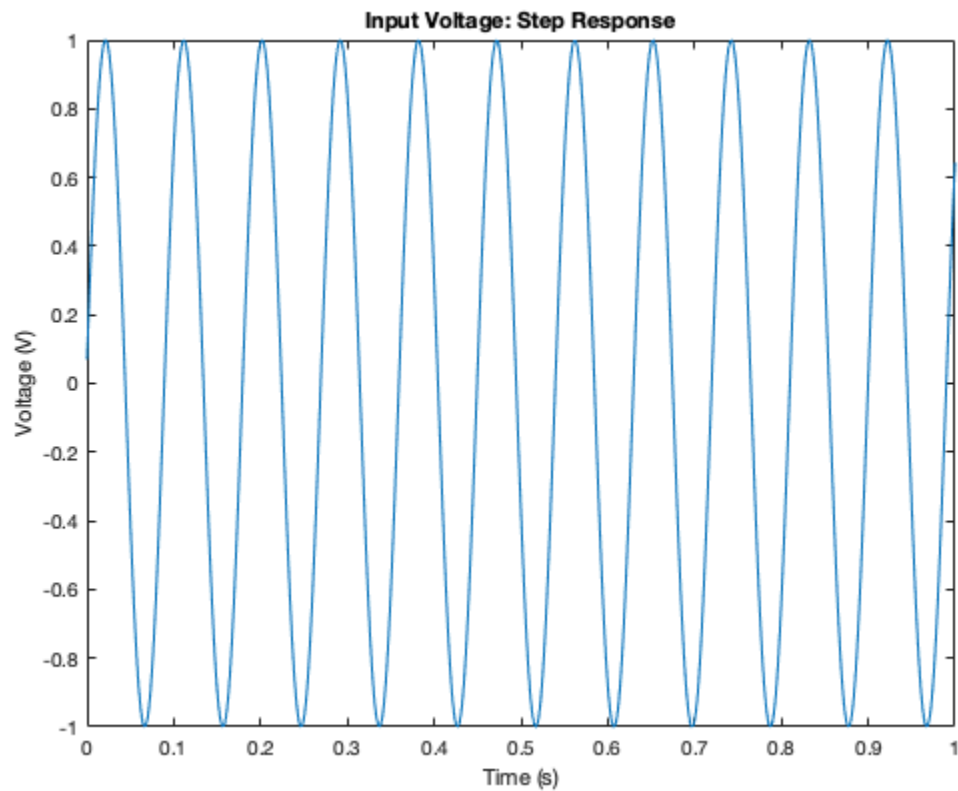

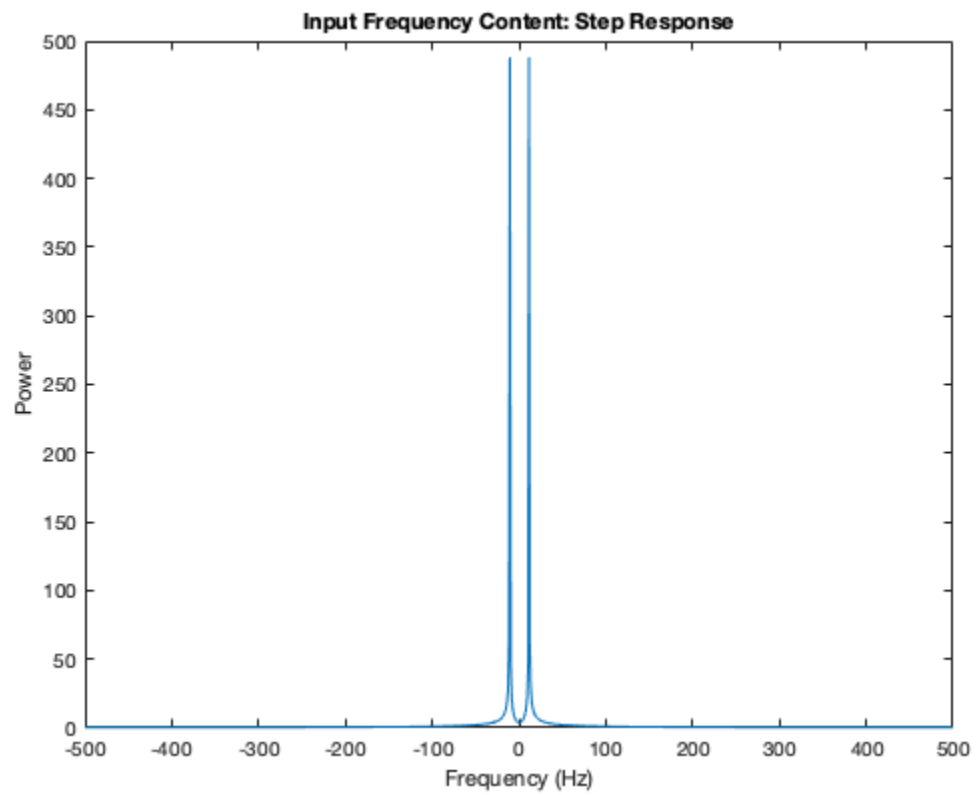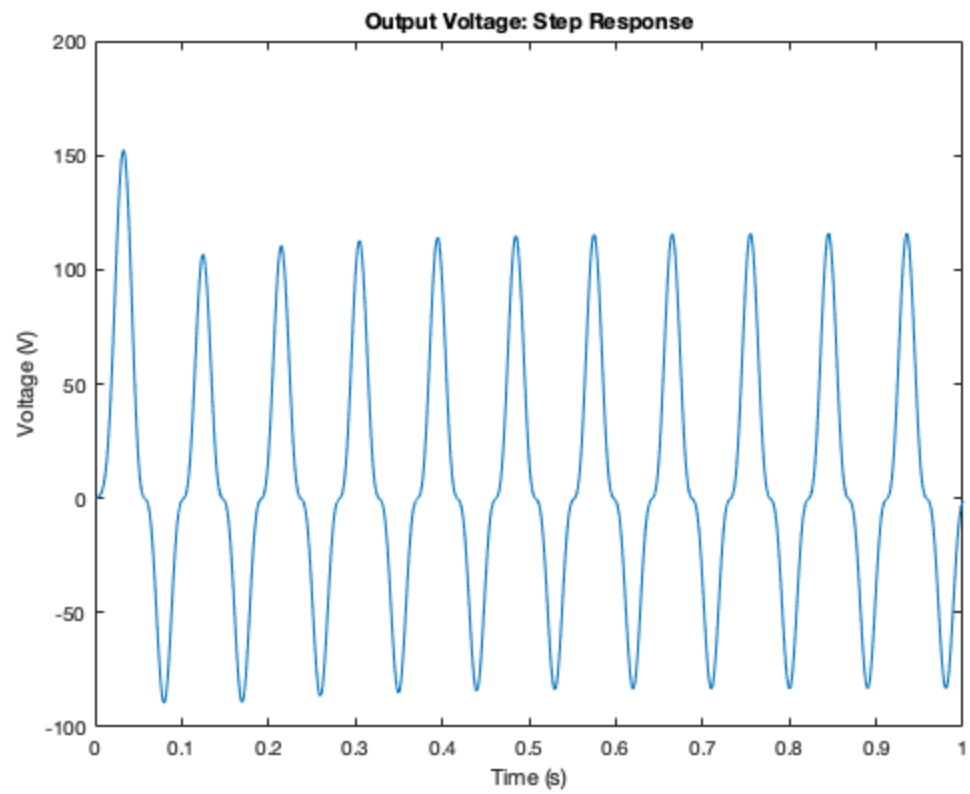

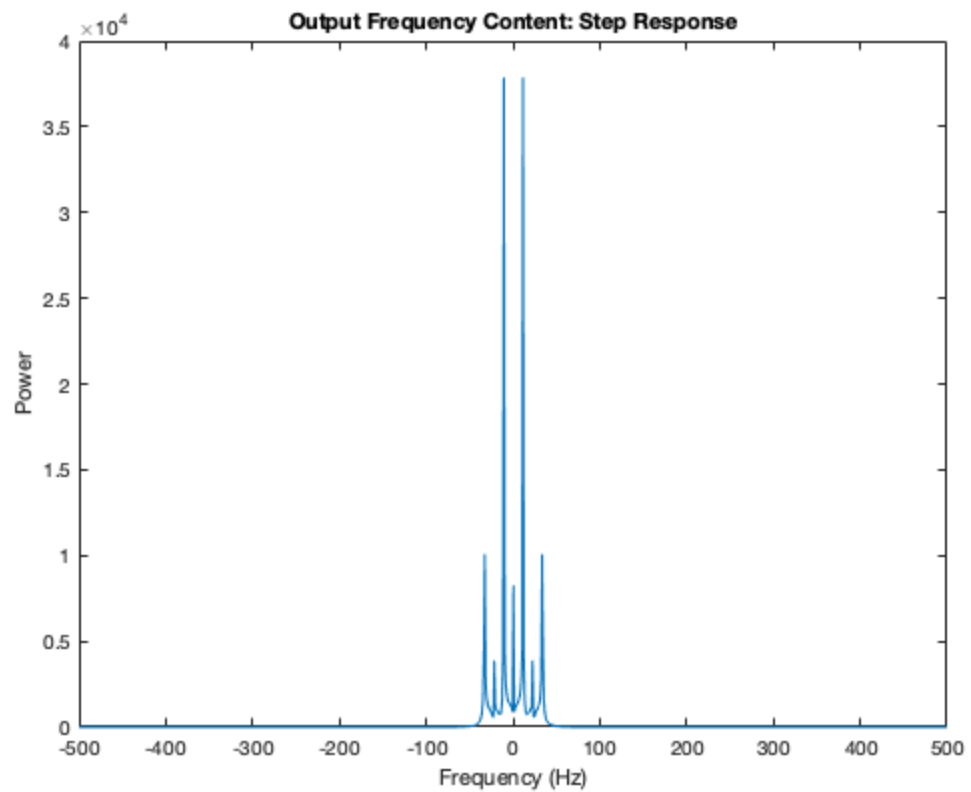

## Conclusion

Overall Assignment 4 was a success. I was able to complete every objective and my results matched my expectation.

*Published with MATLAB® R2018a*